



- Power Supplies
- Bandgap Reference
- Case Study
- Antennas

Power Supply Designs


- AC to DC power supplies *110-240vac 50/60Hz*
 - Linear
 - Switch mode
- DC to DC power supplies *+5v, +14v*
 - Linear
 - Switch mode
- Bandgap reference
- Case study

Power Supply Specifications

- Line regulation: change in output voltage with input change
- Load regulation: change in output voltage with varying load
- Output ripple
- Holdup time
- Input voltage range/frequency
- Efficiency
- Power density W/cu in
- Cost watt/\$


Safety

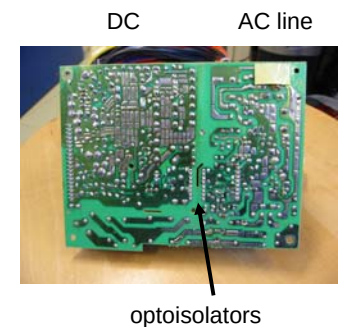- Safety is major issue in power supplies.
- Operation world wide with one design desirable/required
- Input (primary) must be isolated from output (secondary)




350W PC Power Supply

Primary Secondary Isolation

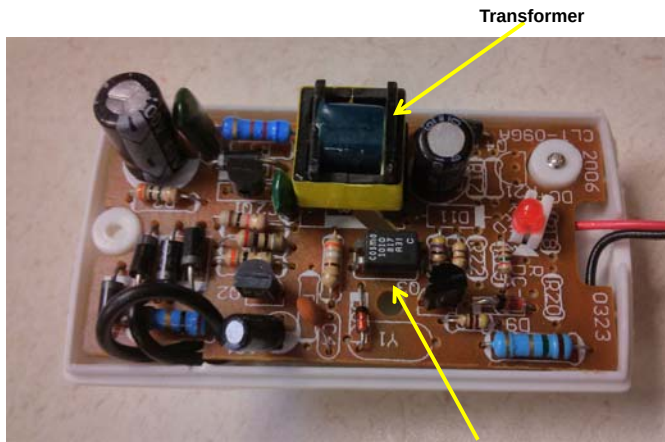

Opto-isolator

Connector Voltage Drop

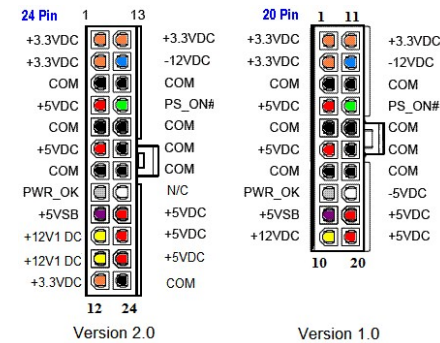

ATX Motherboard power connector

- +12V currents up to 20 amps!
- Voltage drop major issue.
- Solution: additional connectors in parallel
- Must be backwards compatible


AC-DC Power Supply

- Internal: PC power supply
- Brick/Wart: USB charge, cell phone, etc...
- AC input range
 - 100-240VAC (min 92VAC in Japan)
 - 50-60Hz

AC-DC Design Philosophy

- Step down voltage (110-240) at 50/60hz
 - Simple design
 - Large transformer required
- Off-Line Switching
 - Rectify line voltage, step down at 20 - >100kHz
 - Small transformer
 - More complex design
 - Switching noise filter required

Step Down Design Philosophy

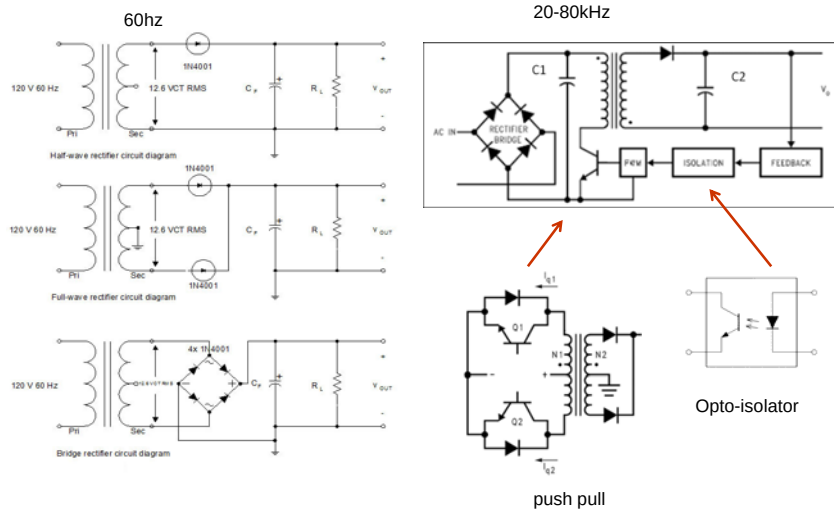


6.101 Spring 2020

Lecture 9

9

Linear Regulator: Zener + BJT

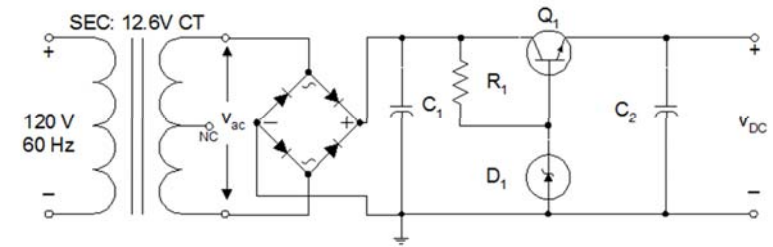


- Simple design
- Output voltage varies (slightly) with current
- Temperature drift
- BJT power dissipation limited
- Low efficiency

6.101 Spring 2020

Lecture 9


10

Linear Voltage Regulator

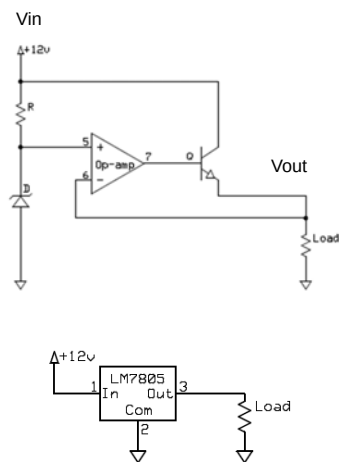

- Simple/low cost design
- Low noise/low ripple
- Fast transient response
- Low dropout voltage
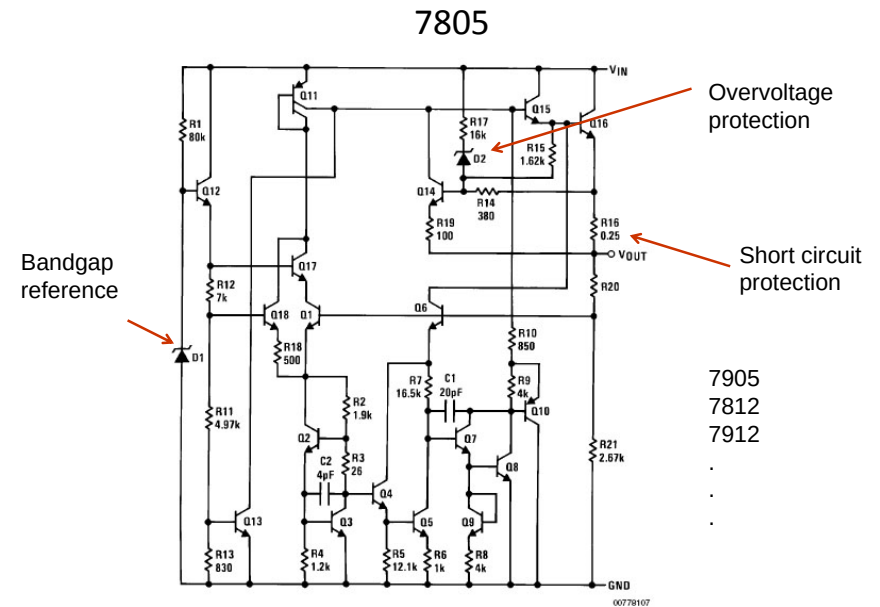
$$\text{Efficiency} = \frac{V_{out} I}{V_{out} I + (V_{in} - V_{out}) I} = \frac{V_{out}}{V_{in}}$$



6.101 Spring 2020

Lecture 9


11

6.101 Spring 2020

Lecture 9

12


LM317

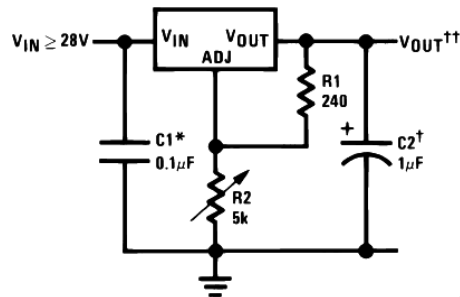

*Needed if device is more than 6 inches from filter capacitors.
 †Optional—improves transient response. Output capacitors in the range of 1 μ F to 1000 μ F of aluminum or tantalum electrolytic are commonly used to provide improved output impedance and rejection of transients.

$$\dagger\dagger V_{OUT} = 1.25V \left(1 + \frac{R2}{R1} \right) + I_{ADJ}(R2)$$

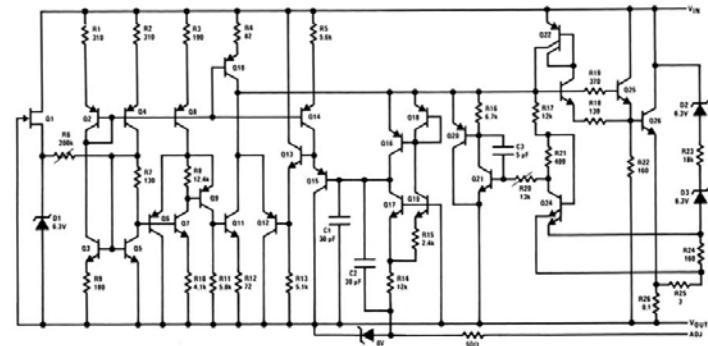LM317 – Three Terminal Adjustable Regulator



- First 3 terminal adjustable voltage regulator
- 1.2 - 25 Voltage output range
- Short circuit protected
- Thermal shutdown


Switching Regulators

- Buck converter – step down converter
- Boost converter – step up
- Flyback converter
- Can be used to generate multiple voltages from single source.
- *Extremely efficient*


Inductor Capacitor Behavior

- Current through an inductor cannot be changed instantly. Since $V = L(di/dt)$, a step change in i would imply an infinite voltage.
 - Result: The current through an inductor just before the switching equals the current just after.
- Steady state voltage across an ideal inductor must be zero. A steady state voltage would imply a constant, nonzero di/dt which results in infinite current.
 - Result: In equilibrium, the voltage across an ideal inductor is zero. (real inductors have resistance which will lead to an IR drop) .
- Voltage across a capacitor cannot be changed instantly. Since $i=C(dv/dt)$ a step change in V would imply an infinite current .
 - Result: the voltage before the switching or pulse equals the voltage just after.
- Steady state current in a capacitor must be zero. A steady state current would integrate to an infinite charge and infinite voltage.
 - Result: in the steady state the average current into a capacitor is zero.

Voltage Schemes

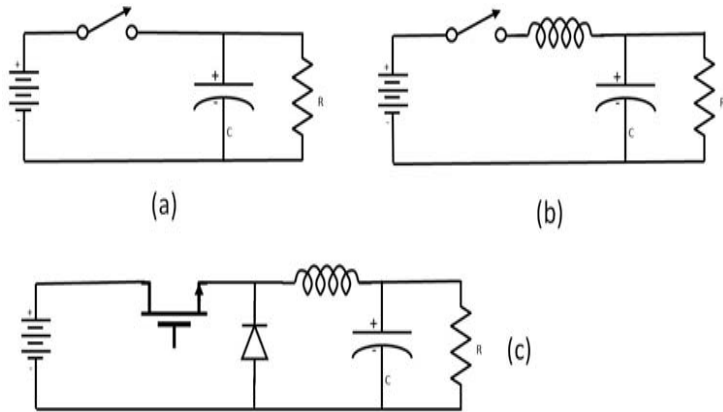


Buck Converter* with MOSFET

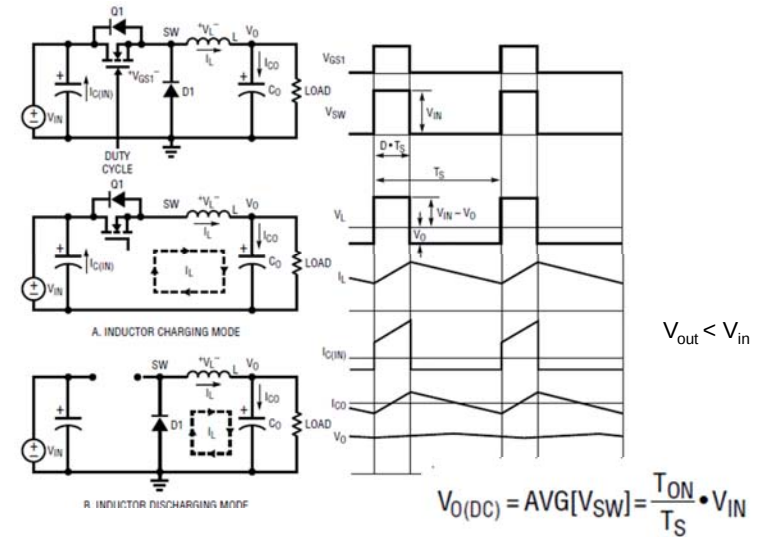

* Linear.com Appnote AN140-1

Buck Converter

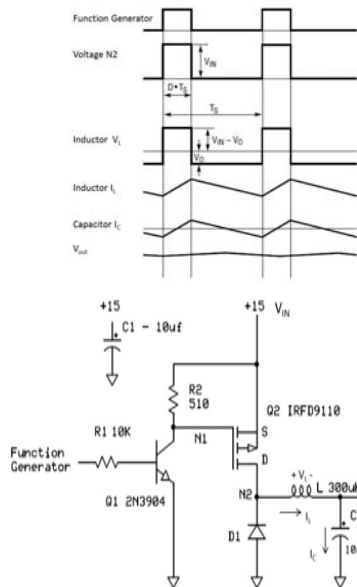

$$v_L(t) = L \frac{di_L(t)}{dt} \quad i_L(t) = i_L(T_o) + \frac{1}{L} \int_{T_o}^T v_L(t) dt$$

At steady state, the current are the same at every T_s or


$$i_L(T_o + T_s) = i_L(T_o) \quad \text{or} \quad i_L(T_o + T_s) - i_L(T_o) = 0 = \frac{1}{L} \int_{T_o}^{T_o + T_s} v_L(t) dt$$

Therefore: average voltage across an inductor must be zero

$$v_{L(\text{average})} = T_{ON} \cdot (v_{IN} - v_O) + (T_s - T_{ON}) \cdot (-v_O) = 0$$

$$\therefore v_O = \frac{T_{ON}}{T_s} v_{IN} \quad D = \frac{T_{ON}}{T_s} \text{ (duty cycle)}$$

Inverting Converter

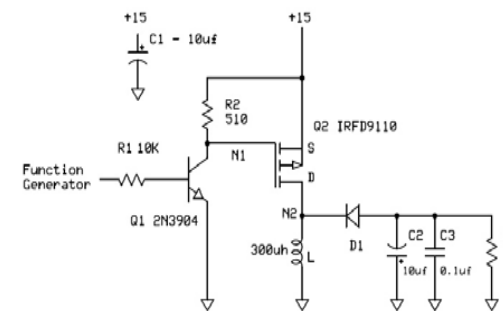


- The current following into the inductor when the MOSFET is on is: $i_L(\text{on}) = \frac{v_{in}}{L} T_{ON}$
- When the MOSFET is off, the diode is conducting; the change in inductor current is

$$i_L(\text{off}) = \frac{v_O}{L} (T_s - T_{ON})$$

- In equilibrium, they are equal and opposite

$$\therefore v_O = -\frac{T_{ON}}{T_s - T_{ON}} v_{IN} = \frac{T_{ON}}{T_{OFF}} v_{IN} \quad \text{with } T_{OFF} = T_s - T_{ON}$$

Boost Converter* with BJT

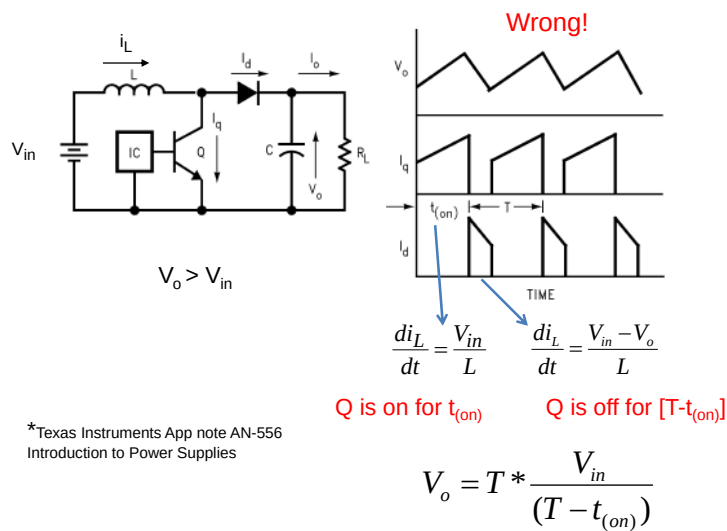

*Texas Instruments App note AN-556
Introduction to Power Supplies

6.101 Spring 2020

Lecture 9

21

Continuous Conduction Mode



- For light loads or low switch frequencies, the current in the inductor can fall to zero.
 - MOSFET and diode become capacitive forming a RLC circuit
- Requires more detailed analysis and design in the feedback and regulation loop.

$$f > (1-D) \left(\frac{V_o}{2i_o L} \right)$$

$$D = \left(\frac{T_{ON}}{T_S} \right)$$

6.101 Spring 2020

Lecture 9

22


Integrated Circuit Solutions

LTC3619 - 400mA/800mA Synchronous Step-Down DC/DC with Average Input Current Limit

Features

- Programmable Average Input Current Limit: $\pm 5\%$ Accuracy
- Dual Step-Down Outputs: Up to 96% Efficiency
- Low Ripple ($< 25mV_{P-P}$) Burst Mode Operation: $I_{CQ} = 50\mu A$
- Input Voltage Range: 2.5V to 5.5V
- Output Voltage Range: 0.6V to 5V
- 2.25MHz Constant-Frequency Operation
- Power Good Output Voltage Monitor for Each Channel
- Low Dropout Operation: 100% Duty Cycle
- Independent Internal Soft-Start for Each Channel
- Current Mode Operation for Excellent Line and Load Transient Resp
- $\pm 2\%$ Output Voltage Accuracy
- Short-Circuit Protected
- Shutdown Current $\leq 1\mu A$
- Available in Small Thermally Enhanced 10-Lead MSE and 3mm $\times$ 3mm DFN Packages

Typical Application

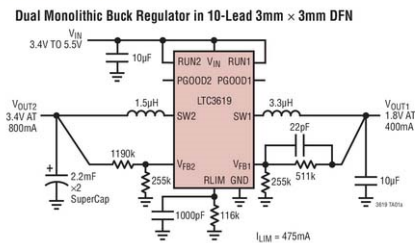


6.101 Spring 2020

Lecture 9

23

Integrated Solutions



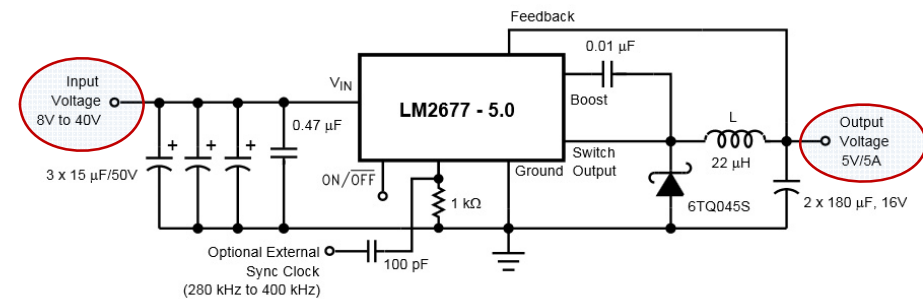


6.101 Spring 2020

Lecture 9

24

Auto USB Charger

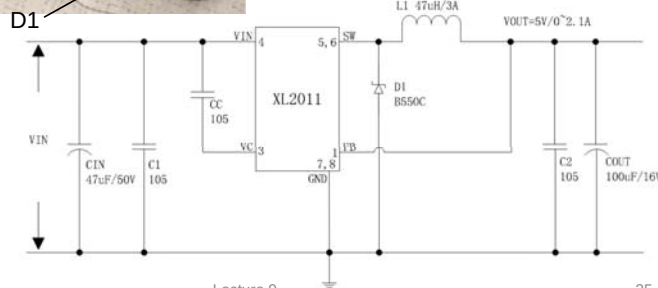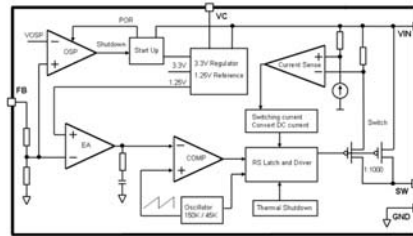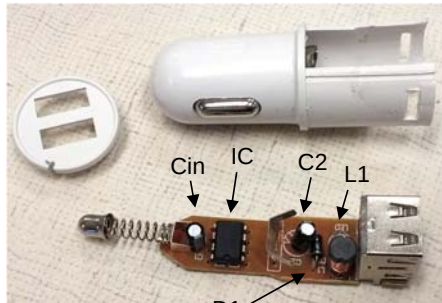

Capacitor
 $104 = 10 \times 10^4 \text{ pf}$
 $= 0.1 \mu\text{f}$

6.101 Spring 2020

Lecture 9

25



Hot Universal Auto Practical Car Charger Dual USB Fast Charging Adapter

Condition: **New**

Color: blue

Quantity: 1 3 available [26 sold / See feedback](#)

Price: **C \$1.24**
 Approximately US \$0.92

[Buy It Now](#)

[Add to cart](#)

[Add to watch list](#)

100% buyer satisfaction

26 sold

More than 53% sold

Shipping: **FREE** Economy Shipping from China/Hong Kong/Taiwan to worldwide | [See details](#)

6.101 Spring 2020

Lecture 9

26

XLSEMI

Datasheet

5V/2.1A 150KHz 45V Buck DC to DC Converter For USB Interface

XL2011

Features

- Wide 8V to 45V input voltage range.
- Fixed 5V output voltage.
- Maximum 2.1A output current.
- Fixed 150KHz switching frequency.
- Internal optimize power MOSFET.
- High efficiency up to 92%.
- Built in output short shutdown function.
- Excellent line and load regulation.
- Built in thermal shutdown function.
- Built in current limit function.

General Description

The XL2011 is a 150 KHz fixed frequency PWM buck (step-down) DC/DC converter, capable of driving a 2.1A load with high efficiency, low ripple and excellent line and load regulation. Requiring a minimum number of external components, the regulator is simple to use and include internal frequency compensation and a fixed-frequency oscillator.



Auto Charger IC

FOB Price: **US \$0.06 / Piece**
 Min. Order: **1 Piece**

Transport Package: **Carton**
 Payment Terms: **T/T, Paypal**

[Contact Now](#)



6.101 Spring 2020

Lecture 9

27

Flyback Converter

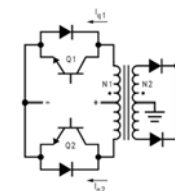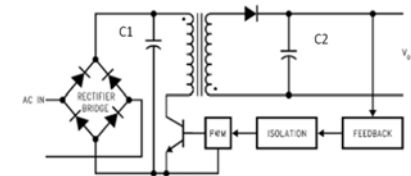- Typically used in off-line switching regulator
- Single or push pull transistor configuration
- Transformer size approximately inversely proportional to frequency.
- Multiple output voltages possible.
- Isolation between primary and secondary absolutely essential.
- EMI line filtering necessary





6.101 Spring 2020

Lecture 9


28

5V - 3.3V Converters

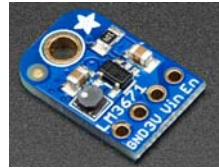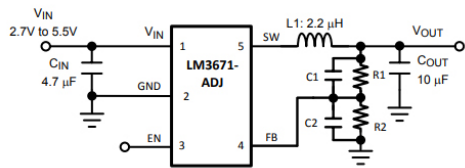- 5VDC – existing standard for digital logic and USB
- 3.3V new standard embedded logic
 - Linear regular: LDO LM1117
 - Buck converter LM3671





USB C

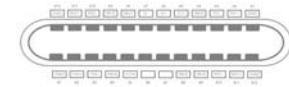

- Universal connector for power and data – first product MacBook Air – one and only port!
- Symmetrical – no orientation (Good for 10,000 insert/withdrawals)
- Supports DisplayPort, HDMI, power, USB, and VGA. Uses differential bidirectional serial communications
- Supplies up to 100W power
- Voltage dictated by software handshake, etc..
- Downside: new adapters required for DisplayPort, HDMI, power, USB, and VGA

USB C - Power Profiles

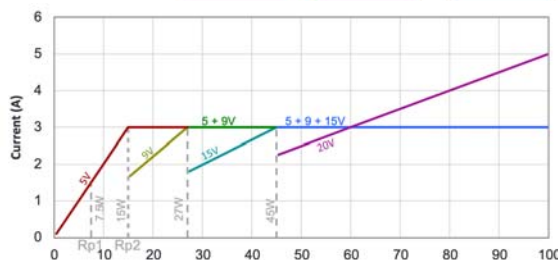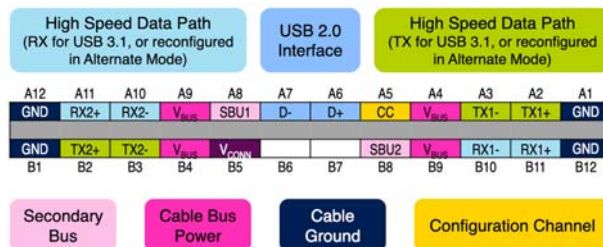


(Source: Figure 10-2 in the USB PD Specification v3.0)

www.st.com/content/ccc/resource/sales_and_marketing/presentation/product_presentation/group0/5a/b1/8e/6c/2b/0d/46/3c/Apec/files/AP_EC_2016_USB_Power.pdf/_jcr_content/translations/en.APEC_2016_USB_Power.pdf


Band Gap Reference

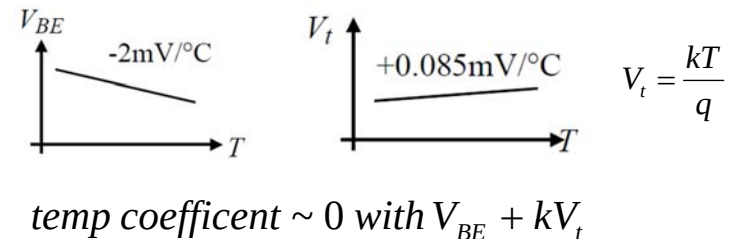- Conceptualize by David Hibiber 1964
- Realized/implemented by Bob Widlar 1971
- Summed voltage = 1.25 (silicon bandgap voltage)*



*bandgap: amount of energy needed to free an electron from its orbit to become a mobile charge carrier.



LM309 Bandgap

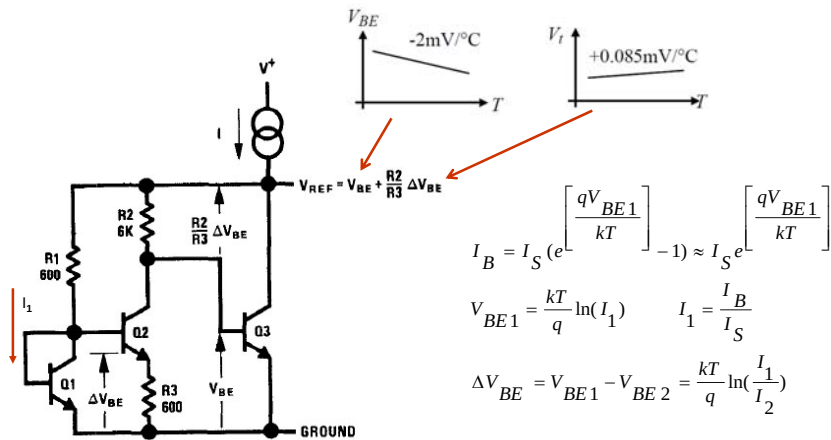

Widlar, Robert J. (February 1971), "New Developments in IC Voltage Regulators", IEEE Journal of Solid-State Circuits 6 (1): 2-7, doi:10.1109/JSSC.1971.1050151

Case Study TI-5500 I/O Expander

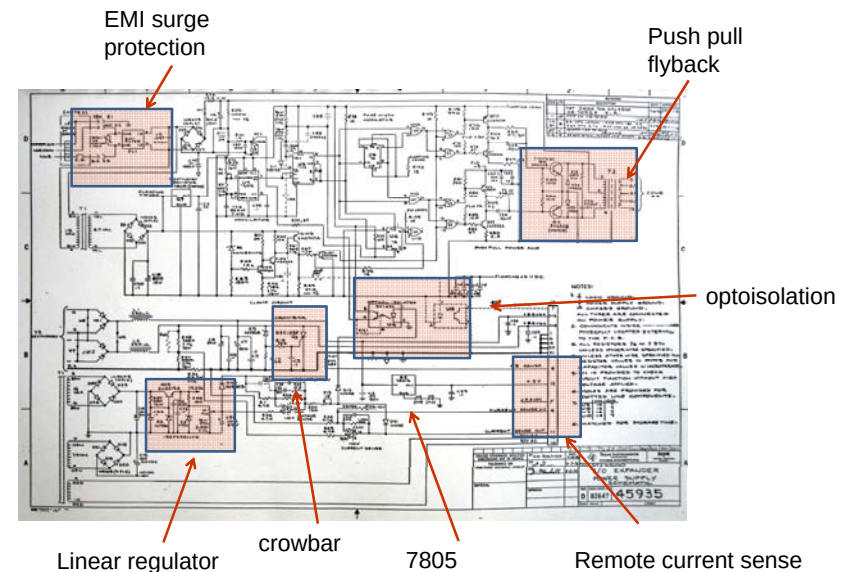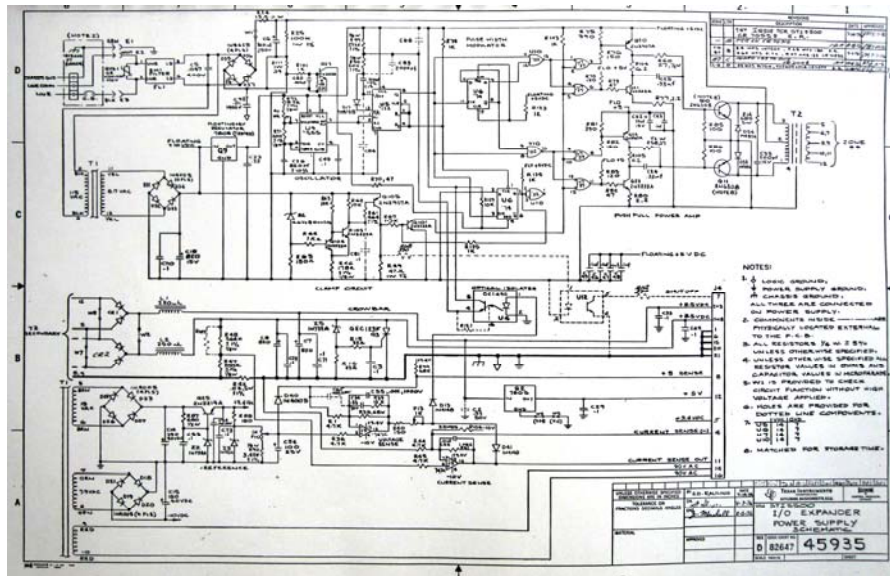- Power supply for control system
- Input: 90-120VAC 50-60Hz
- Output
 - (2) 8.5V 15 amp
 - 5V 1 amp
 - Undervoltage sense
 - Overvoltage shutdown
 - Overcurrent protection



Walk Through



- Heat sink
- EMI
- MOV
- Opto-isolation
- Crowbar
- Fast recovery diodes
- Low ESR capacitors
- Hi Pot

Black Heatsinks

- Property: *emissivity*
Highly polished (shiny, white) objects have low emissivity, black object have high emissivity.
- Black surfaces absorb heat better, but it also radiates it better.
- The SR-71 Blackbird is black for radiative heat transfer – cooler than unpainted. At Mach 3.5 air is heating up the plane.



EMI Filter

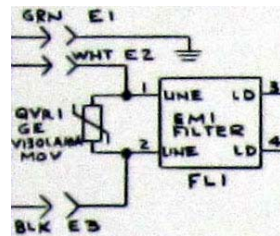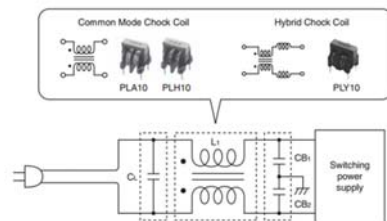

Symbol	Name	Function
L_1	Common mode choke coil	Suppresses common mode noise
C_L	Across the line capacitor (X-capacitor)	Suppresses differential mode noise
CB_1 CB_2	Line bypass capacitor (Y-capacitor)	Suppresses common mode noise and differential mode noise

<http://www.murata.com/products/catalog/pdf/c35e.pdf>

MOV

- Metal Oxide Varistor
- Zinc Oxide + other metal oxide forming small multiple back to back diodes
- Specs:
 - energy rating in joules,
 - operating voltage,
 - response time,
 - maximum current,
 - breakdown (clamping) voltage.
- Key component in surge protectors



Littlefuse MOV

Absolute Maximum Ratings

• For ratings of individual members of a series, see Device Ratings and Specifications chart

Continuous		TMOV® and iTMOV® Series	Units
Steady State Applied Voltage:			
AC Voltage Range (V_{ACRMS})		115 to 750	V
Transient:			
Peak Pulse Current (I_{PP}) - For 8x20µs Current Wave, single pulse		6,000 to 10,000	A
Single-Pulse Energy Capability - For 2ms Current Wave		35 to 480	J
Operating Ambient Temperature Range (T_A)		-55 to +85	°C
Storage Temperature Range (T_{stg})		-55 to +125	°C
Temperature Coefficient (αV) of Clamping Voltage (V_C) at Specified Test Current		<0.01	%/°C
Hi-Pot Encapsulation (COATING Isolation Voltage Capability)		2,500	V
Thermal Protection Isolation Voltage Capability (when operated)		600	V
COATING Insulation Resistance		1,000	MΩ
Indicator Lead Rating (Lead-3 - iTMOV® varistor only):			
Continuous RMS current		100	mA
Surge Current, 8/20µs		10,000	A

CAUTION: Stresses above those listed in "Absolute Maximum Ratings" may cause permanent damage to the device. This is a stress only rating and operation of the device at these or any other conditions above those indicated in the operational sections of this specification is not implied.

TMOV and iTMOV® Ratings & Specifications


TMOV Lead-free And RoHS Compliant Models		iTMOV Lead-free and RoHS Compliant Models		Disc Diameter	Maximum Rating (85°C)				Specifications (25°C)				
Part Number	Branding	Part Number	Branding		Continuous		Transient		Varistor Voltage at 1mA Test Current	Maximum Clamping Voltage 8/20µs	V_{CL} Min	V_{CL} Max	Typical Capacitance (f = 1MHz)
				AC Volts	DC Volts	Energy 2ms	Peak Surge Current 8/20µs						
					V_{ACRMS}	V_{DC}	W_{2ms}	I_{PP} 1 x Pulse	I_{PP} 2 x Pulse	V_{AKS} Min	V_{AKS} Max	V_{CL}	C
				(mm)	(V)	(V)	(J)	(A)	(A)	(V)	(V)	(A)	(pF)
TMOV14RP115E	P4T115E	TMOV14RP115M	P4T115M	14	115	150	35	6000	4500	162	198	300	50
TMOV20RP115E	P2T115E	TMOV20RP115M	P2T115M	20	115	150	52	10000	6500	162	198	300	100
TMOV14RP130E	P4T130E	TMOV14RP130M	P4T130M	14	130	170	50	6000	4500	184	226	340	50
TMOV20RP130E	P2T130E	TMOV20RP130M	P2T130M	20	130	170	100	10000	6500	184	226	340	100
TMOV14RP150E	P4T150E	TMOV14RP150M	P4T150M	14	150	200	65	10000	6500	206	250	380	50
TMOV20RP150E	P2T150E	TMOV20RP150M	P2T150M	20	150	200	100	10000	6500	206	250	380	100

6.101 Spring 2020

Lecture 9

41

Push Pull Flyback

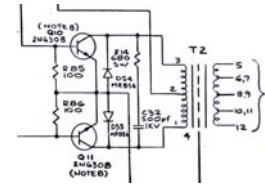

Description:

High voltage, TO-3, NPN, Silicon, Power Transistor. Designed for high voltage inverters, switching regulators and line - operated amplifier applications. Especially well suited for switching power supply applications in associated consumer products.

Features:

- Low Collector Emitter Saturation Voltage: $V_{CE(sat)}$ 1.5V(Max.) @ I_C - 3A
- Current Gain-bandwidth Product: 5MHz (Min.) @ I_C - 0.3A

Absolute Maximum Ratings:

Collector-Base Voltage, V_{CB0}	: 700V
Collector-Emitter Voltage, V_{CE0}	: 350V
Emitter-Base Voltage, V_{EB0}	: 8V
Continuous Collector Current, I_C	: 8A
Base Current I_B	: 4A
Total Device Dissipation (T_C = +25°C), P_D	: 125W
Densite above 25°C	: 0.714mW/°C
Operating Junction Temperature Range, T_J	: -55°C to +200°C
Storage Temperature Range, T_{stg}	: -55°C to +200°C

Electrical Characteristics: (T_A = +25°C unless otherwise specified)

Parameter	Symbol	Test Conditions	Min.	Max.	Unit
OFF Characteristics					
Collector-Emitter Breakdown Voltage	$V_{BR(CEO)}$	$I_C = 100mA, I_B = 0$	350	-	V
Collector Cut-Off Current	I_{CIX}	$V_{CE} = 700V, V_{EB(sat)} = 1.5V$	-	0.5	mA
Emitter Cut-Off Current	I_{EBO}	$V_{CB} = 350V, I_B = 0$	-	0.5	mA
ON Characteristics (Note 1)					
DC Current Gain	β_{FE}	$V_{CE} = 5V, I_C = 3A$	12	60	-
		$V_{CE} = 5V, I_C = 8A$	3	-	-
Collector-Emitter Saturation Voltage	$V_{CE(sat)}$	$I_C = 3A, I_B = 0.6A$	-	1.5	V
		$I_C = 8A, I_B = 2.67A$	-	5	V
Base-Emitter Saturation Voltage	$V_{BE(sat)}$	$I_C = 8A, I_B = 2.67A$	-	2.5	V
Base-Emitter On Voltage	$V_{BE(on)}$	$I_C = 3A, V_{CE} = 5V$	-	1.5	V

High breakdown voltage

Low beta



6.101 Spring 2020

Lecture 9

42


Optoisolators

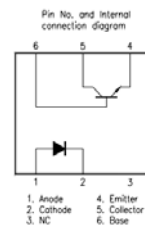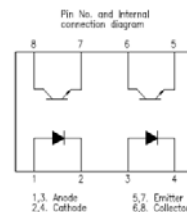- Electrically isolate circuits in two voltage domains
- Isolator achieved through vacuum or air gap
- Typical isolation: 5000 volts rms



- Circuit to protect against overvoltage failure
- Overvoltage triggers SCR/TRIAC
- Relies on overcurrent protection or fuse.

Crowbar

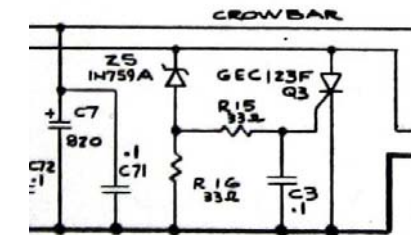

6.101 Spring 2020

Lecture 9


43

6.101 Spring 2020

Lecture 9

44

Fast Recovery Diodes

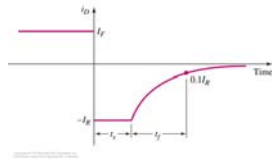

Fast recovery times achieved by manipulating doping levels and junction geometry

Description	General Purpose Rectifier	Fast Switching Rectifier	Small Signal Diode	Schottky Diode
Sample Device	1N4001	1N4933	1N4148	ZC2800
Maximum DC/Average Forward Current	1 A	1 A	300 mA	15 mA
Maximum Reverse Voltage	50 V	50 V	75 V	70 V
Reverse Leakage Current @ 25 °C and V _R = 20 V	50 nA	200 nA	5 nA	200 nA
Forward Voltage	~0.7 V	1 V @ I _F = 1 A	1 V @ I _F = 10 mA	0.41 V @ 1 mA
Reverse Recovery Time	2 μs	200 ns	4 ns	1 ns
Cost	20 cent	15 cent	25 cent	100 cent

Low ESR Capacitors




Equivalent circuit for the high-frequency

Re: Electrode resistance
Rd: ESR due to dielectric loss
Ri: Insulation resistance

- ESR – Equivalent Series Resistance
- Electrolytic 10μf: 0.1-3Ω
- Ceramic, low ESR: <0.015Ω

Hi Pot

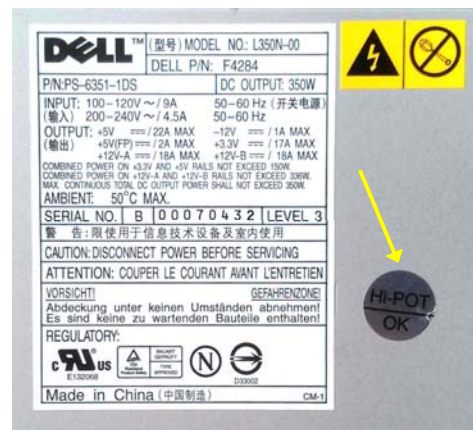- Safety test to verify isolation between primary and secondary.
- High potential test



Switching Power Supply Losses


- Inductor loss
- Capacitor ESR loss
- Diode loss
- BJT/MOSFET conduction loss
- BJT/MOSFET rise/fall time loss
- Gate drive loss

Antennas

Goals

- To show the possibility of harvesting energy from the environment, and in the case of our lab from the radio station antennas on top of the Prudential center.
- To gain basic understanding of how antennas work and how to use the Friis transmission equation.
- To make an interesting analog circuit that uses the harvested energy to perform a task.

Overview of Prudential Center Antennas

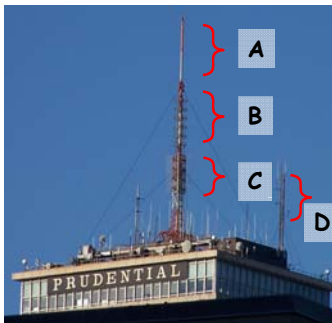

<http://www.necrat.us/prudential.html>




<https://www.fybush.com/sites/2004/site-040709.html>



The first TV broadcasting antennas were mounted on the Prudential tower in October 1964. FM radio antennas came a few years later.

Overview of Prudential Radios

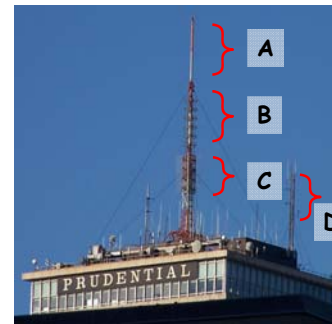



<http://www.necrat.us/prudential.html>

D: backup antenna

Antenna	Frequency (MHz)	Power (kW)	Center of radiation (m)
B	100.7	21.5	235
	1004.1	21.0	
	106.7	21.5	
	107.9	20.5	
C	92.90	18.5	224
	105.7	23.0	
	96.90	22.5	

Stations	100.7:	 WZLX Classic Rock
	105.7:	 WROR Classic Hits

How Far Are We from the Tower?

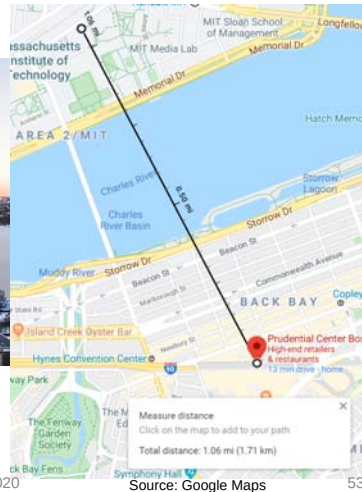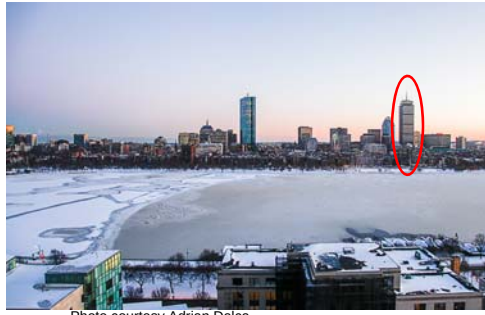


6.101 Spring 2020

53


Antenna Basics

Isotropic Antenna

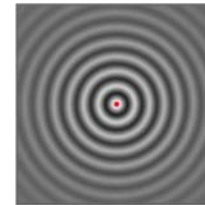An isotropic antenna is a hypothetical antenna radiating the same intensity of radio waves in all directions.




Source: Wikipedia

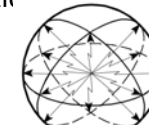

Source: Mathworks

Directional Antenna

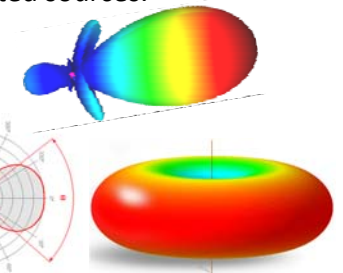An antenna which radiates or receives greater power in specific directions allowing increased performance and reduced interference from unwanted sources.




Source: <https://www.radartutorial.eu/>

6.101 Spring 2020

54

Antenna Polarization

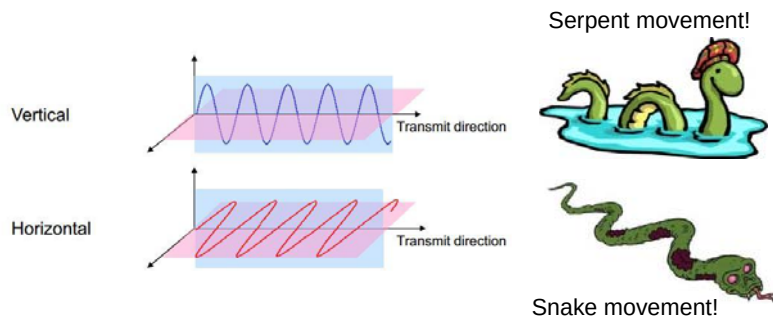- Electric field can be either vertical or horizontal (or a combination of both).



Source: Google Photos


6.101 Spring 2020

55

Monopole Antenna



Source: arcantenna.com

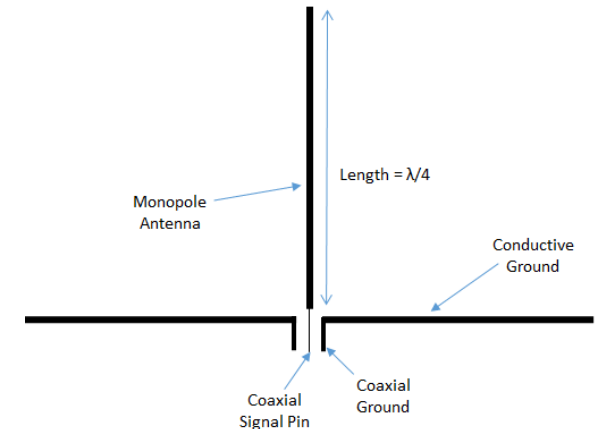


Source: microwavetools.com

6.101 Spring 2020

56

Example WiFi Router Antennas

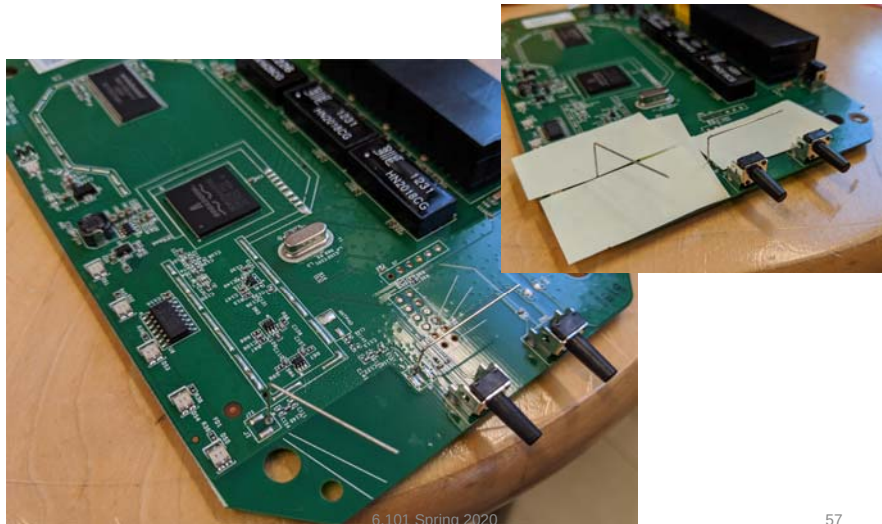

57

Antenna Directivity

- Antenna Gain (G) describes how much power is transmitted in the direction of radiation to that of an isotropic source.
- Usually reported in dBi unit.


$$G_{dBi} = 10\log_{10}(G)$$

6.101 Spring 2020


58

Half-wave (Dipole) Antenna

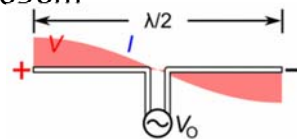- For the 96.9MHz channel, λ is = 3.096m
- So $\frac{\lambda}{2} = \frac{c}{2f} = 154.8\text{cm}$
- Directivity Gain: 2.15dBi ($G = 1.64$)



Radiation Pattern of a dipole antenna:

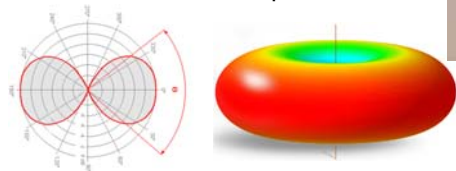

6.101 Spring 2020


59

Other Types of Antennas

Horn Antenna




Patch Antenna

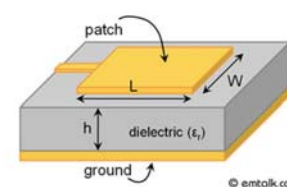


Source: Google Photos

Inverted-F Antenna

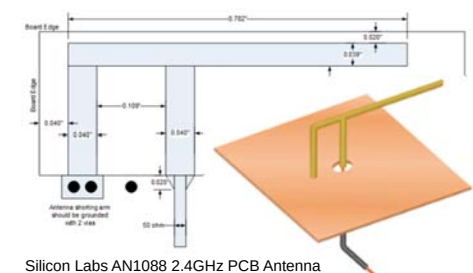


Silicon Labs AN1088 2.4GHz PCB Antenna

Slot Antenna

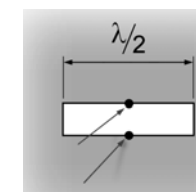

6.101 Spring 2020

Yagi-Uda Antenna

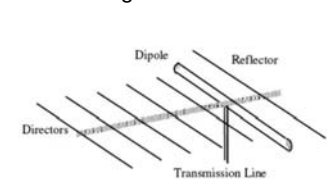


60

Prudential Tower Antenna Gain

- Let's assume the tower is equipped with an isotropic hemisphere antenna.
- Meaning that the radiated power is isotopically distributed in half the sphere.
- This means
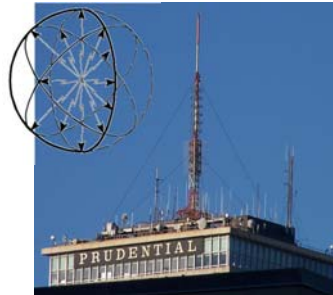
$$G_{dBi} = 10\log_{10}(2) = 3\text{dBi}$$



6.101 Spring 2020

61

Friis Transmission Equation

- The “Friis Transmission Equation” is used to calculate the power received from one antenna (with gain G_r), when transmitted from another antenna (with gain G_t), separated by a distance r , and operating at wavelength λ .

$$P_r = G_t G_r P_t \left(\frac{\lambda}{4\pi r} \right)^2$$

6.101 Spring 2020

62

Power we can receive at MIT?

- For a transmitted power of 22.5kW (see above), we can receive:


$$P_r = G_t G_r P_t \left(\frac{\lambda}{4\pi r} \right)^2$$

$$P_r = 2 \times 1.64 \times 22.5 \times 10^3 \times \left(\frac{3.096}{4\pi \times 1700} \right)^2 \approx 1.55 \text{ mW}$$

Prudential Center



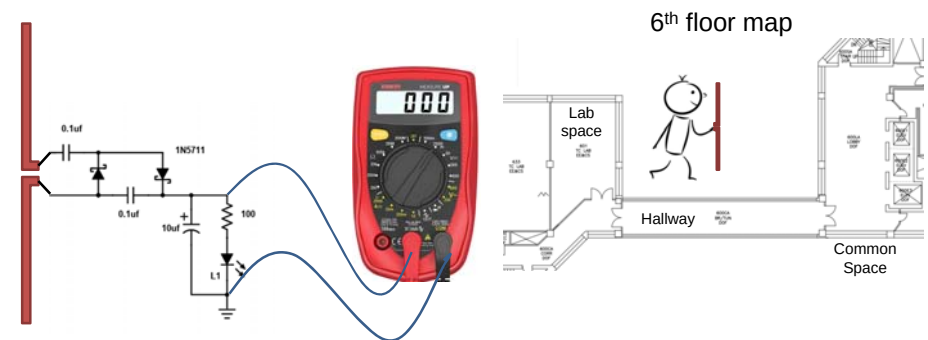Find the Optimal Spot to Maximize Your Reading



Answer the following questions:

- What polarization would maximize your reading?
- What location would maximize your reading?
- What is the maximum voltage that you can read?

6.101 Spring 2020

64



What Else Can We Do?

- With this power harvester design an interesting circuit:
 - Flashing light
 - Generating a beep
 - Activating a buzzer
- Please note that the higher the power required, the bigger the capacitor and the longer the charging time for the capacitor.